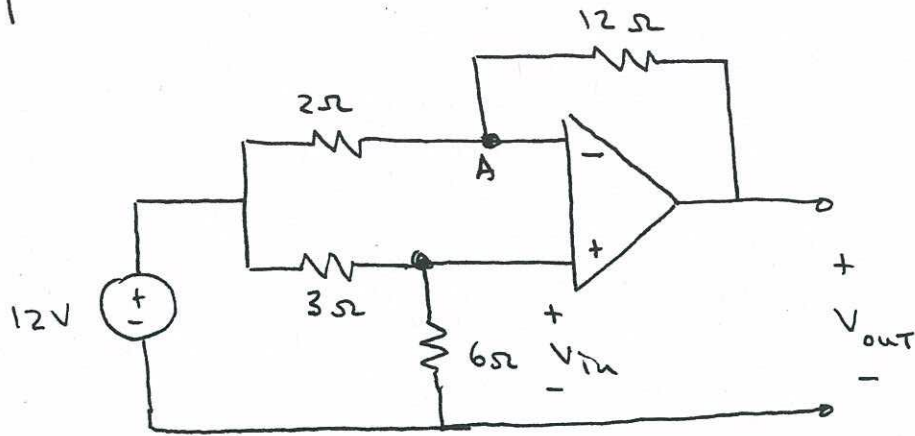


5.1



$$V_{in} = \left(\frac{6\Omega}{3\Omega + 6\Omega} \right) 12V = 8V$$


Op-amp rules: $V_A = V_{in} = 8V$

KCL at node A:

$$\frac{12V - V_{in}}{2\Omega} = \frac{V_{in} - V_{out}}{12\Omega} \Rightarrow \frac{12V - 8V}{2\Omega} = \frac{8V - V_{out}}{12\Omega}$$

$$V_{out} = -16V$$

5.2

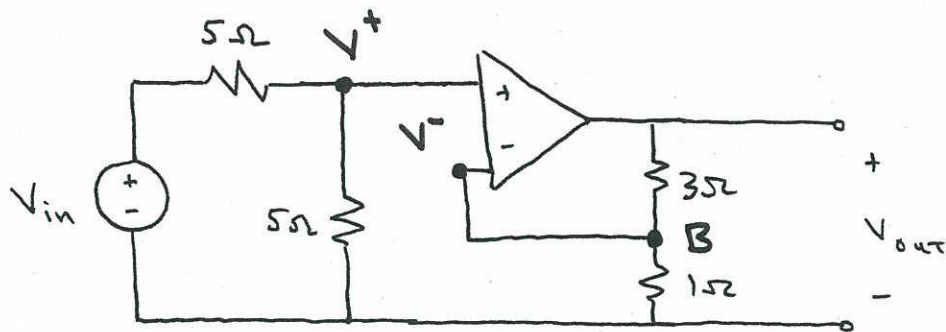

$$V^+ = \left(\frac{5\Omega}{5\Omega + 5\Omega} \right) V_{in} = \frac{V_{in}}{2}$$


Op-amp rules: $V^- = V^+ = \frac{V_{in}}{2}$

KCL at B:

$$\frac{V_B}{1\Omega} = \frac{V_{out} - V_B}{3\Omega} \Rightarrow \frac{V_{in}}{2} = \frac{V_{out} - \frac{V_{in}}{2}}{3}$$

$$V_{out} = 2 V_{in}$$

5.3

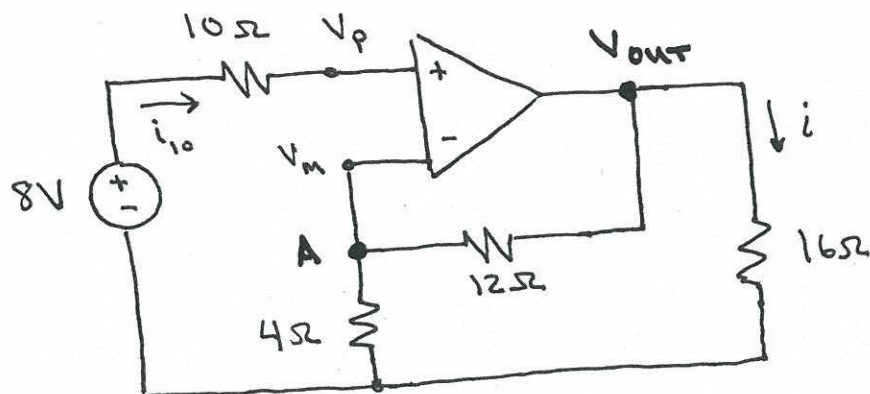

Apply op-amp rules:


$$i_{10} = 0 \Rightarrow V_p = 8V$$

$$V_p = V_m \Rightarrow V_m = 8V$$

$$\text{KCL at "A": } \frac{8V}{4\Omega} = \frac{V_{OUT} - 8V}{12\Omega} \Rightarrow V_{OUT} = 32V$$

$$\text{Ohm's Law: } i = \frac{V_{OUT}}{16\Omega} = \frac{32V}{16\Omega} \Rightarrow \boxed{i = 2A}$$

5.4

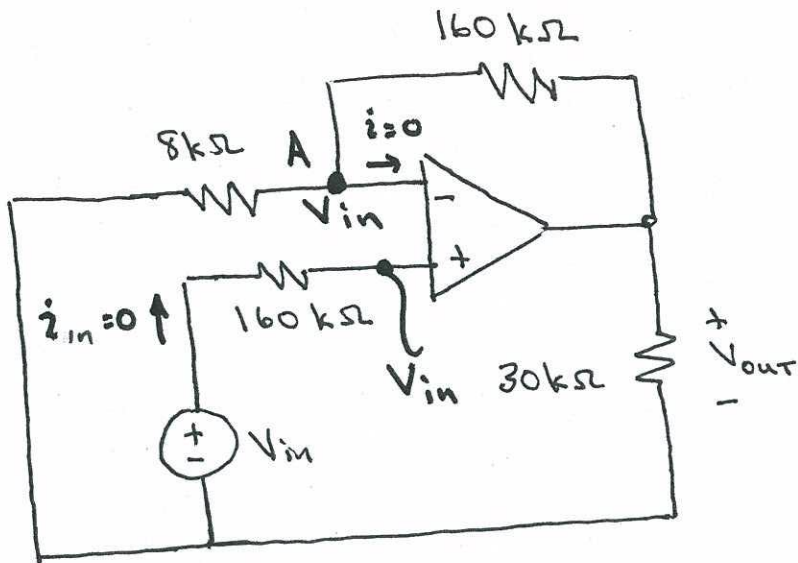

Op-Amp rules:

$$i_{in} = 0 \Rightarrow V_{in} = V_p$$

$$V_p = V_n = V_{in}$$


KCL at A:

$$\frac{0 - V_{in}}{8 \text{ k}\Omega} = \frac{V_{in} - V_{out}}{160 \text{ k}\Omega} \Rightarrow -20 V_{in} = V_{in} - V_{out}$$

$$V_{out} = 21 V_{in}$$

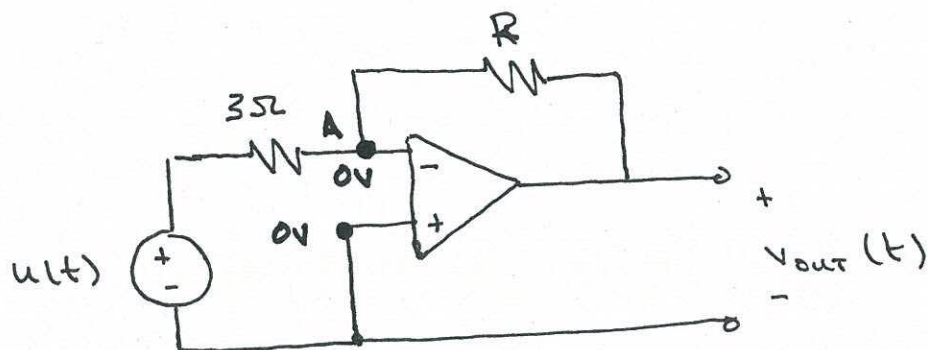5.5

Probably easiest to find an input-output relation, and apply both inputs to that:



$$R = \frac{(8\Omega)(24\Omega)}{8\Omega + 24\Omega} = 6\Omega$$

Equivalent resistance of parallel 8Ω & 24Ω resistors

KCL at A: $\frac{u(t) - 0}{3\Omega} = \frac{0 - v_{out}(t)}{R} \Rightarrow 2u(t) = -v_{out}(t)$


$v_{out}(t) = -2u(t)$

(a)

$$v_{out}(t) = -2[4V] \Rightarrow \boxed{v_{out}(t) = -8V}$$

(b) $v_{out}(t) = -2[2\cos(5t)] \Rightarrow \boxed{v_{out}(t) = -4\cos(5t) V}$

5.6

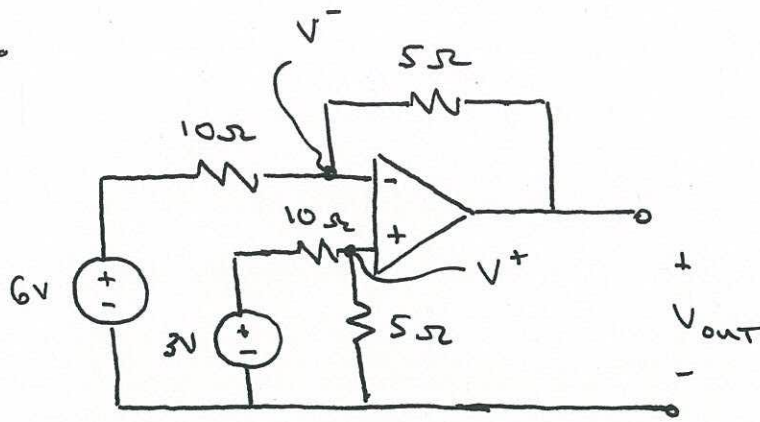

Non-inverting input: $\frac{3V - V^+}{10\Omega} = \frac{V^+ - 0V}{5\Omega} \Rightarrow V^+ = 1V$

Opamp rules $\Rightarrow V^- = V^+ \Rightarrow V^- = 1V$

KCL at inverting input:


$$\frac{6V - V^-}{10\Omega} = \frac{V^- - V_{OUT}}{5\Omega}$$

$$\frac{6V - 1V}{10\Omega} = \frac{1V - V_{OUT}}{5\Omega}$$

$$5V = 2V - 2V_{OUT}$$

$$\underline{\underline{V_{OUT} = -\frac{3}{2} V}}$$

5.7

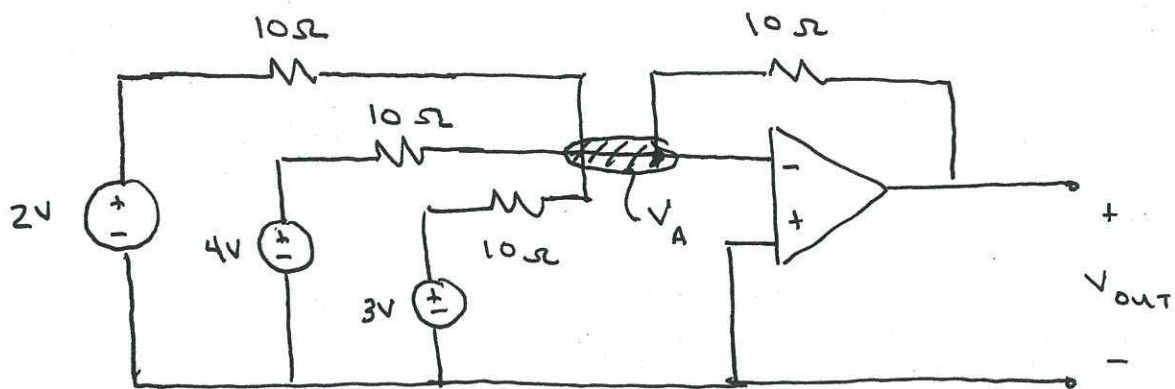

Op-amp rules: $V_A = 0V$


KCL at node A:

$$\frac{2V - V_A}{10\Omega} + \frac{4V - V_A}{10\Omega} + \frac{3V - V_A}{10\Omega} = \frac{V_A - V_{out}}{10\Omega}$$

$$\frac{2V}{10\Omega} + \frac{4V}{10\Omega} + \frac{3V}{10\Omega} = -\frac{V_{out}}{10\Omega}$$

$$\underline{\underline{V_{out} = -9V}}$$

5.8

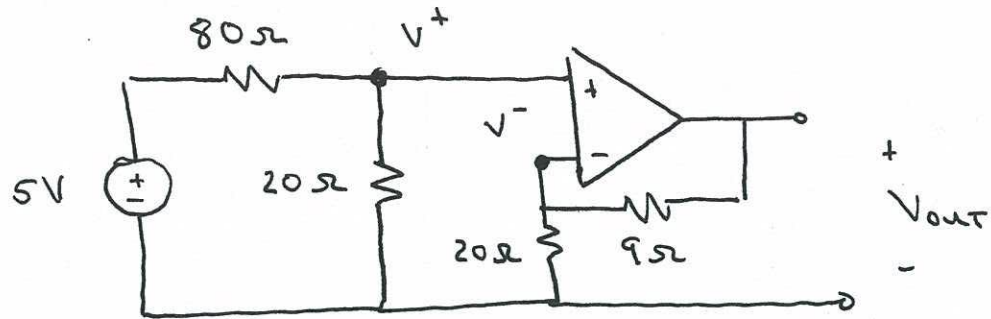

KCL at non-inverting input:

$$\frac{5V - V^+}{80\Omega} = \frac{V^+ - 0V}{20\Omega} \Rightarrow V^+ = 1V$$

Op-amp rules: $V^- = V^+ \Rightarrow V^- = 1V$


KCL at inverting input:

$$\frac{V^- - 0V}{20\Omega} + \frac{V^- - V_{out}}{9\Omega} = 0$$

$$\frac{1V}{20\Omega} + \frac{1V - V_{out}}{9\Omega} = 0$$

$$\underline{\underline{V_{out} = \frac{29}{20} V}}$$

5.9

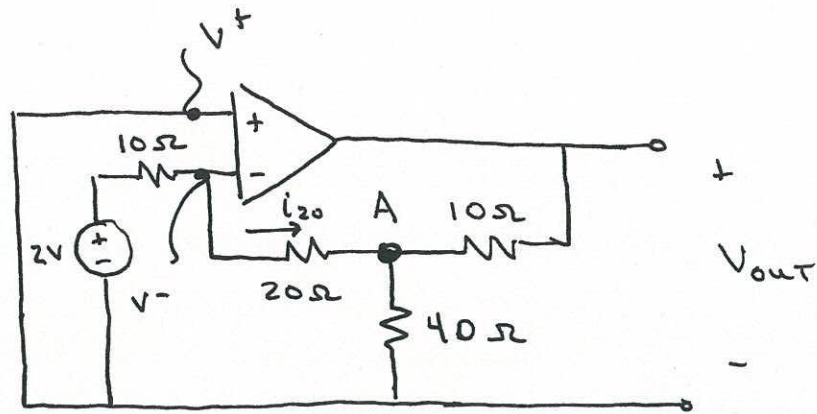

$$V^+ = 0 \Rightarrow V^- = 0 \quad (\text{op-amp rules})$$

KCL at A:

$$\frac{V_A - V^-}{20\Omega} + \frac{V_A - 0V}{40\Omega} + \frac{V_A - V_{out}}{10\Omega} = 0$$


$$\frac{V_A}{20\Omega} + \frac{V_A}{40\Omega} + \frac{V_A}{10\Omega} = \frac{V_{out}}{10\Omega} \Rightarrow V_{out} = \frac{7}{4} V_A$$

KCL at inverting input:

$$\frac{2V - V^-}{10\Omega} = i_{20} \Rightarrow i_{20} = \frac{1}{5} A$$

$$\text{Ohm's Law: } V^- - V_A = (20\Omega) i_{20} \Rightarrow V_A = -4V$$

$$\underline{\underline{V_{out} = 7V}}$$

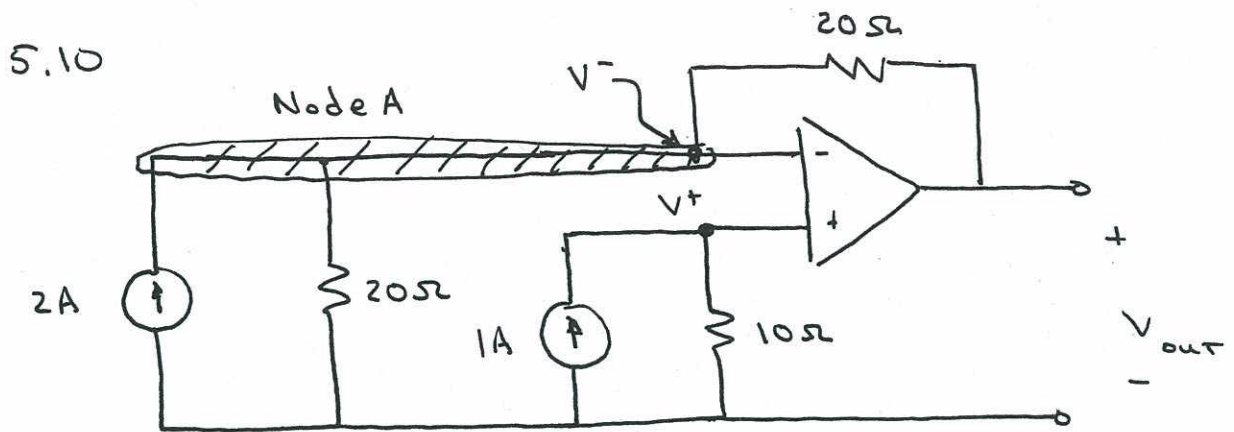

$$V^+ = (10\Omega)(1A) = 10V$$

Op-amp rule: $V^+ = V^- = 10V$

KCL, node A:


$$2A = \frac{V^-}{20\Omega} + \frac{V^- - V_{out}}{20\Omega}$$

$$40V = V^- + V^- - V_{out}$$

$$40V = 10V + 10V - V_{out}$$

$$\underline{\underline{V_{out} = -20V}}$$

5.11

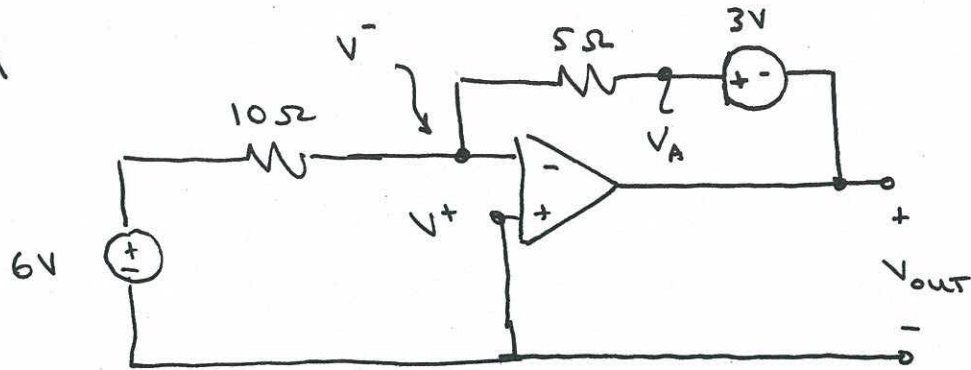

$$V^- = V^+ = 0V \quad (\text{op-amp rules})$$

KCL at inverting input:

$$\frac{6V - V^-}{10\Omega} = \frac{V^- - V_A}{5\Omega} \Rightarrow 6V - V^- = 2V^- - 2V_A$$

$$6V = -2V_A$$


$$V_A = -3V$$

$$V_A = V_{out} + 3V$$

$$V_{out} = V_A - 3V$$

$$\underline{\underline{V_{out} = -6V}}$$

5.12

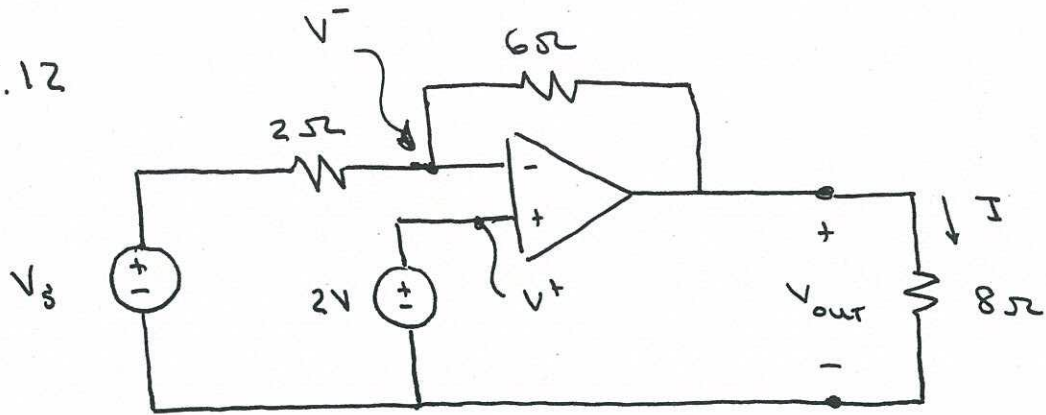

$$V^+ = 2V \Rightarrow V^- = 2V \quad (\text{op-amp rules})$$

KCL at inverting input:

$$\frac{V_s - V^-}{2\Omega} = \frac{V^- - V_{out}}{6\Omega} \Rightarrow 3V_s - 4V^- = V_{out}$$


$$V_{out} = 8V - 3V_s$$

Ohm's Law:

$$I = \frac{V_{out}}{8\Omega}$$

$$I = \underline{\underline{\frac{8V - 3V_s}{8\Omega}}}$$

5.13

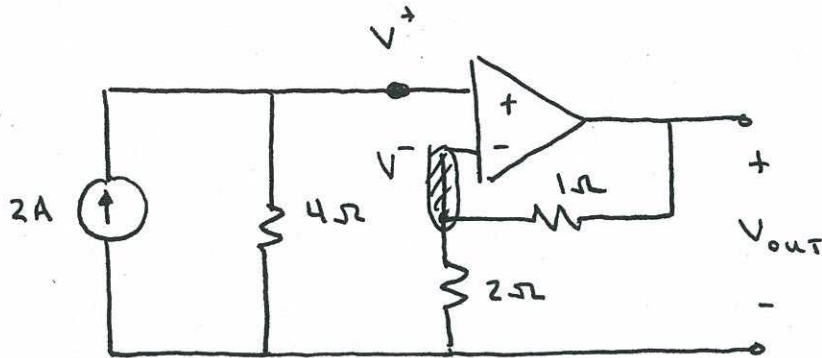

$$V^+ = (2A)(4\Omega) = 8V$$

KCL at inverting input
+ Ohm's law

$$V^- = V^+ = 8V \quad (\text{op-amp rules})$$


KCL at inverting input:

$$\frac{V^- - 0V}{2\Omega} + \frac{V^- - V_{out}}{1\Omega} = 0 \Rightarrow 3V^- = 2V_{out}$$

$$2V_{out} = (3)(8V)$$

$$\underline{\underline{V_{out} = 12V}}$$

5.14

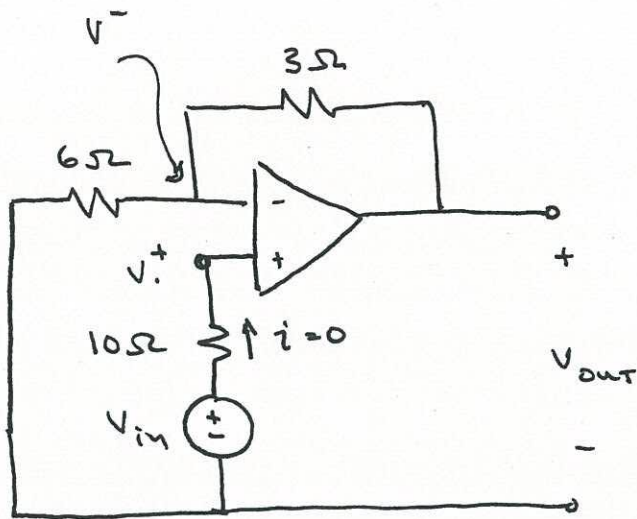

$$V^+ = V_{in}$$

$$V^- = V^+ = V_{in}$$

no current into input terminals, so no voltage drop across 10Ω resistor


KCL at inverting input:

$$\frac{V^- - 0V}{6\Omega} = \frac{V_{out} - V^-}{3\Omega} \Rightarrow 2V_{out} = 3V^-$$

$$2V_{out} = 3(V_{in})$$


$$\underline{\underline{V_{out} = \frac{3}{2} V_{in}}}$$

S.15

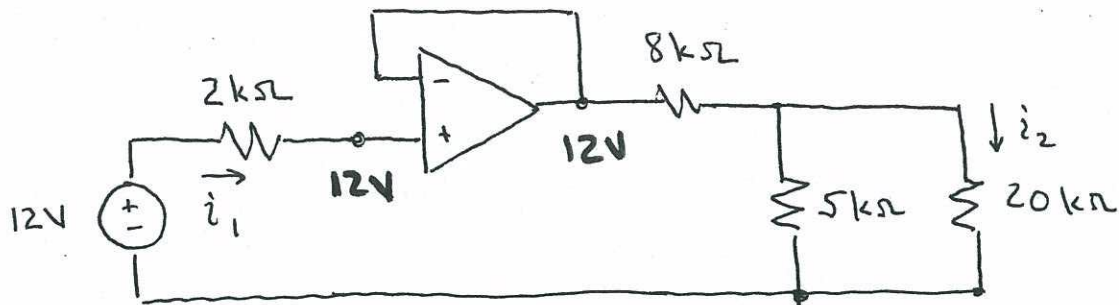


From op-amp rules, $i_1 = 0A$

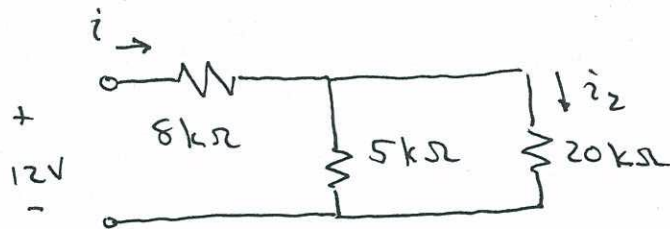From op-amp rules, op-amp output voltage = 12V,
so circuit to determine i_2 is:




↓ Equivalent circuit

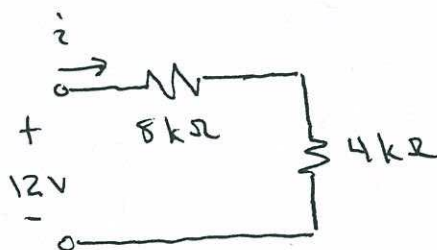

$$\Rightarrow i = \frac{12V}{8k\Omega + 4k\Omega} = 1mA$$


current divider:

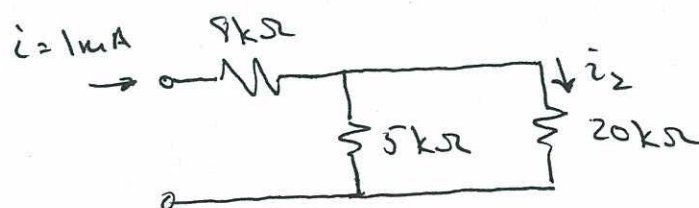

$$i_2 = \frac{5k\Omega}{5k\Omega + 20k\Omega} (1mA)$$

$$i_2 = 0.2mA$$

5.16

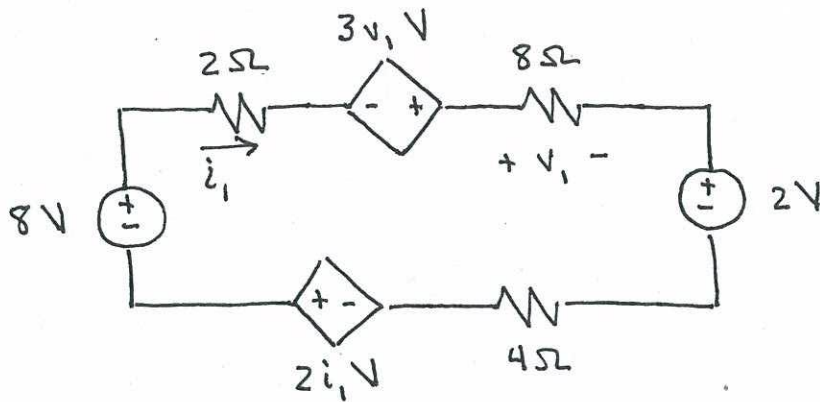

KVL :


$$-8V + (2\Omega) i_1 - 3v_1 + v_1 + 2V + (4\Omega) i_1 - 2i_1 = 0$$

$$v_1 = (8\Omega) i_1$$

$$-6 - 2v_1 + \frac{v_1}{2} = 0 \Rightarrow -3v_1 = 12$$

$$v_1 = -4V$$

5.17

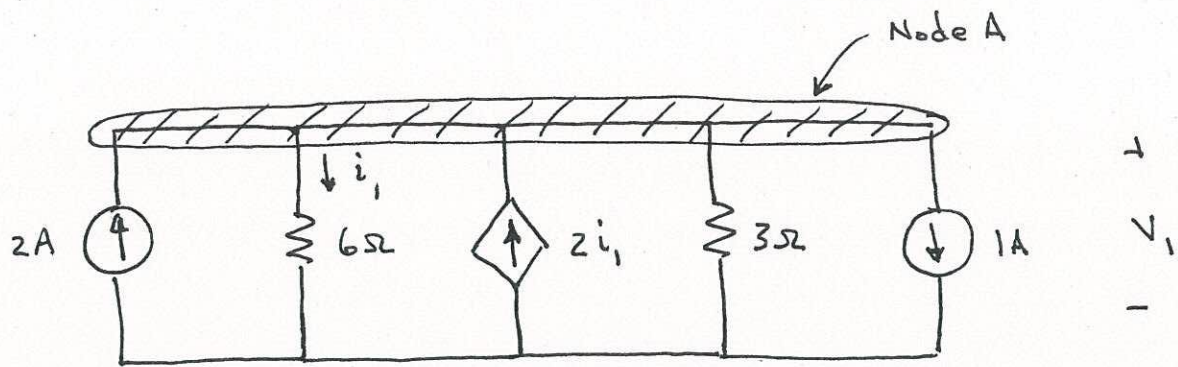

KCL, Node A:

$$-2A + i_1 - 2i_1 + \frac{V_1}{3\Omega} + 1A = 0$$

Ohm's Law:

$$i_1 = \frac{V_1}{6\Omega} \Rightarrow V_1 = 6i_1$$

$$\rightarrow -2 + i_1 - 2i_1 + \frac{6i_1}{3\Omega} + 1 = 0 \Rightarrow \boxed{i_1 = 1A}$$