
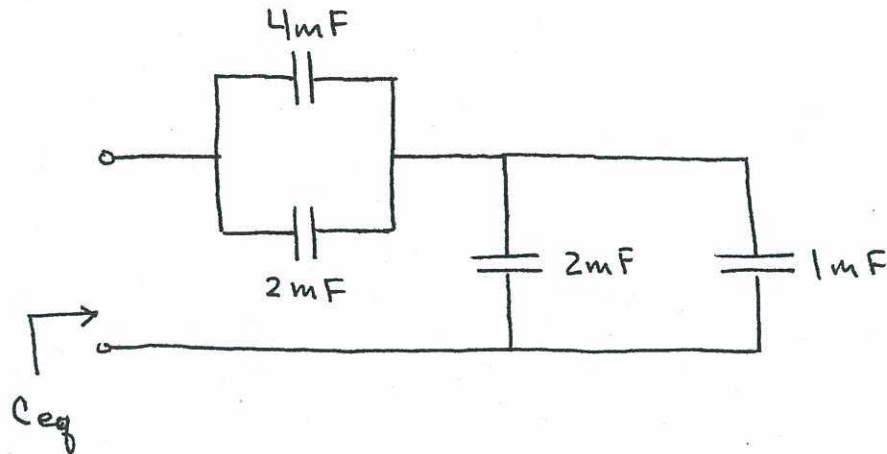


6.1

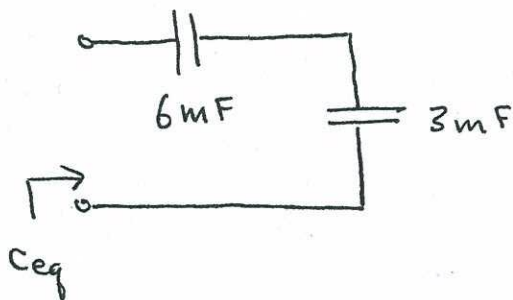



Capacitors in parallel add directly, so the above is equivalent to:



Capacitors in series add like resistors in parallel:

$$C_{eq} = \frac{(3\text{mF})(6\text{mF})}{3\text{mF} + 6\text{mF}} \Rightarrow \boxed{C_{eq} = 2\text{mF}}$$

6.2

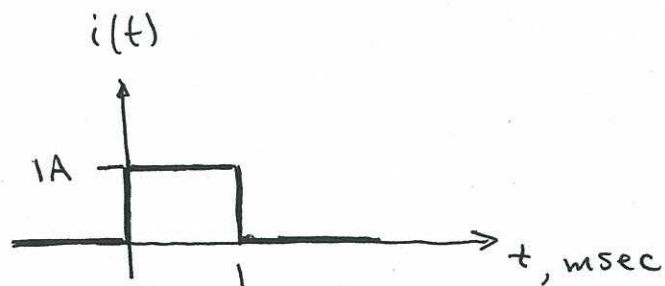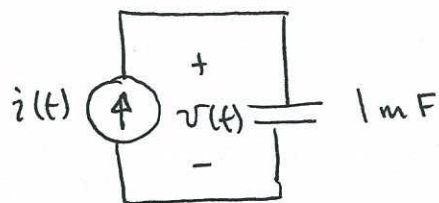


voltage - current relation for capacitors:


$$v(t) = \frac{1}{C} \int_0^t i(t) dt + v(0)$$

0 (capacitor initially uncharged)
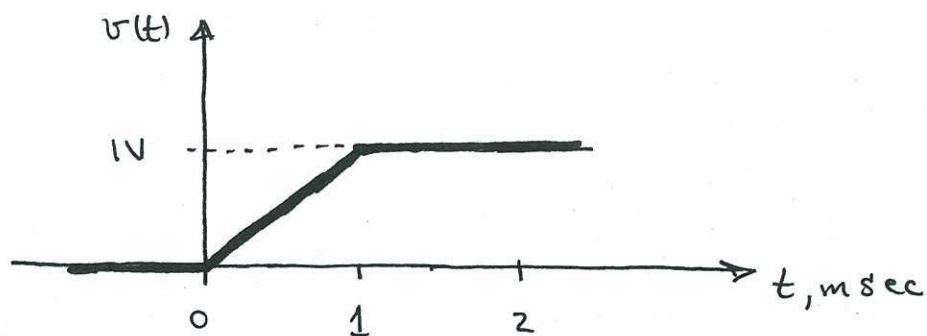
$$v(t) = 1000 \int_0^t 1 dt, \quad 0 < t < 1 \times 10^{-3} \text{ sec}$$




6.3

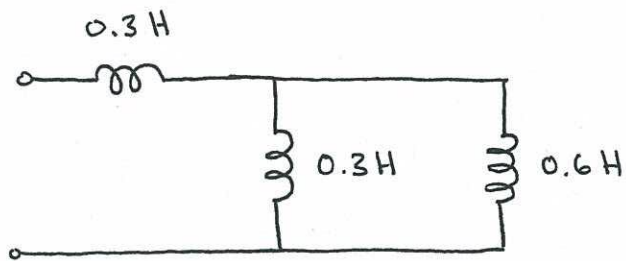

$$L_{eq} = 0.3 \text{ H} + \frac{(0.3 \text{ H})(0.6 \text{ H})}{0.3 \text{ H} + 0.6 \text{ H}}$$

$$L_{eq} = 0.5 \text{ H}$$

6.4

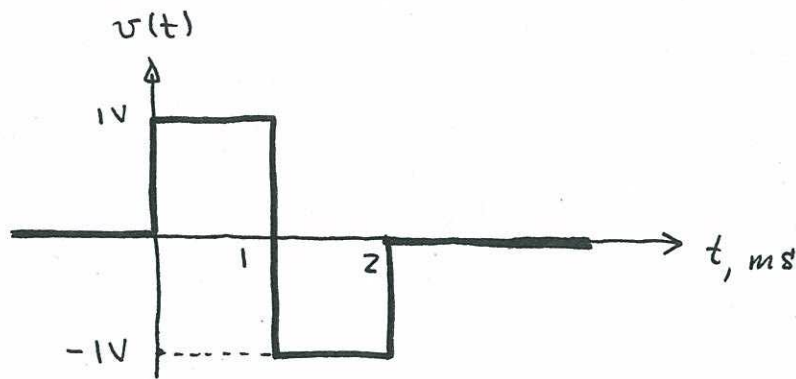

$$L = 1 \text{ mH}$$

Voltage-current relationship:

$$i(t) = \frac{1}{L} \int_0^t v(t) dt + i(t=0)$$

← assume initial current is zero (inductor relaxed at time $t=0$).

