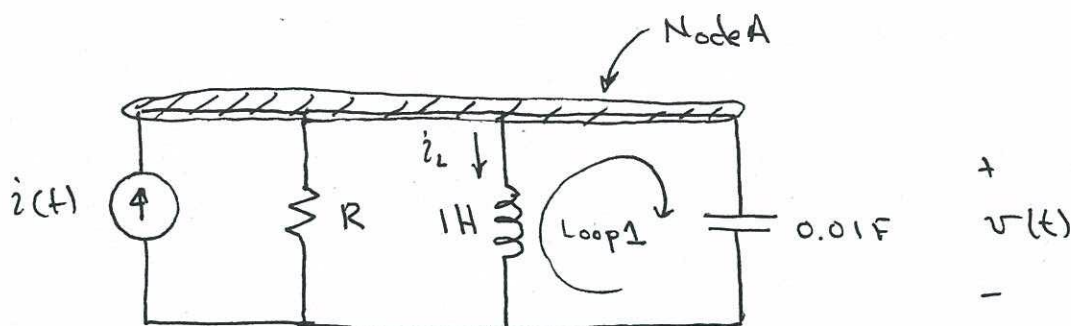


8.1



(a) Define the current through the inductor = $i_L(t)$

$$\text{KCL at node A: } i(t) = \frac{v(t)}{R} + i_L(t) + (0.01F) \frac{dv(t)}{dt} \quad (*)$$

$$\text{KVL, loop 1: } v(t) = (1H) \frac{di_L(t)}{dt} \quad (**)$$

Differentiate equation (*) with respect to time:

$$\frac{di(t)}{dt} = \frac{1}{R} \frac{dv(t)}{dt} + \frac{di_L(t)}{dt} + 0.01 \frac{d^2v(t)}{dt^2}$$

substitute equation (**):

$$100 \frac{di(t)}{dt} = \frac{100}{R} \frac{dv(t)}{dt} + 100 v(t) + \frac{d^2v(t)}{dt^2}$$

(b) From above, $\omega_n^2 = 100 \Rightarrow \omega_n = 10 \text{ rad/sec}$


$$2\zeta\omega_n = \frac{100}{R} \Rightarrow 2(1)(10 \text{ rad/s}) = \frac{100}{R} \Rightarrow R = \underline{\underline{5}}$$

↑
 $\zeta=1$, for critical damping

$$R = 5\Omega$$

8.2

After switch opens, circuit becomes:

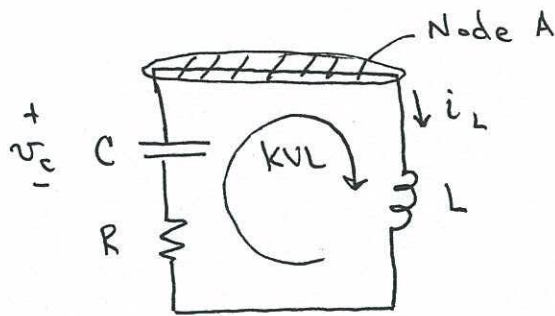

Define two unknowns,
 v_c & i_L

(a) KCL, Node A: $i_L = -C \frac{dv_c}{dt}$

KVL: $v_c + R \frac{dv_c}{dt} = L \frac{di_L}{dt}$

$$\frac{d^2 v_c}{dt^2} + \frac{R}{L} \frac{dv_c}{dt} + \frac{1}{LC} v_c = 0$$

With $R = 2\Omega$, $C = 1\mu F$, $L = 1mH$:


$$\frac{d^2 v_c}{dt^2} + 2000 \frac{dv_c}{dt} + 1 \times 10^9 v_c = 0$$

(b) $\omega_n = \sqrt{1 \times 10^9} = 3.16 \times 10^4 \text{ rad/sec}$

$$\xi = \frac{2000}{2\omega_n} = 0.0316$$

$\xi < 1 \Rightarrow$ System is underdamped

8.3

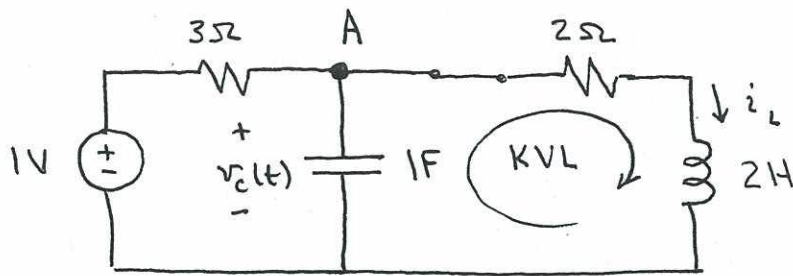

(a) KCL at A: $\frac{1-v_c}{3\Omega} = (1F) \frac{dv_c}{dt} + i_L \Rightarrow 1-v_c = 3 \frac{dv_c}{dt} + 3i_L \quad (*)$

KVL: $v_c = (2\Omega) i_L + (2H) \frac{di_L}{dt} \quad (**)$


Subst. tute (**) into (*):

$$1 = [2i_L + 2 \frac{di_L}{dt}] + 3 \left[2 \frac{di_L}{dt} + 2 \frac{d^2 i_L}{dt^2} \right] + 3i_L$$

$$1 = 5i_L + 8 \frac{di_L}{dt} + 6 \frac{d^2 i_L}{dt^2}$$

(b) Initial condition

Circuit at $t=0^-$:

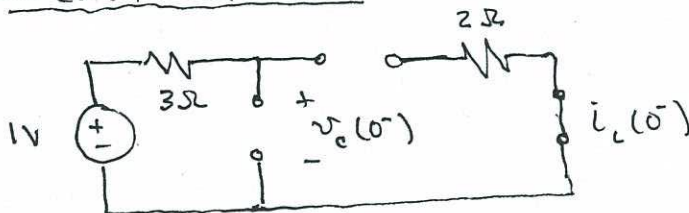


$$v_c(0) = 1V$$

$$i_L(0) = 0A$$

Final Condition:


Circuit at $t \Rightarrow \infty$:

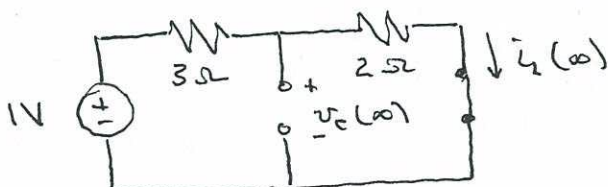

$$v_c(\infty) = \frac{2\Omega}{2\Omega + 3\Omega} = \frac{2}{5} V$$

$$i_L(\infty) = \frac{1V}{5\Omega} = \frac{1}{5} A$$

8.4

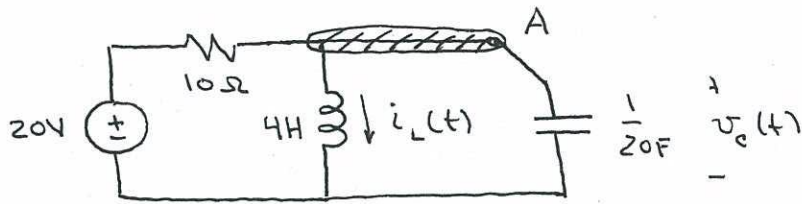(a) For $t > 0$, circuit becomes:KVL, right-most loop: $v_c = 4 \frac{di_L}{dt}$ KCL, node A: $\frac{20 - v_c}{10\Omega} = i_L + \frac{1}{20} \frac{dv_c}{dt}$

Combining:

$$2 - 4 \frac{di_L}{dt} = i_L + \frac{1}{20} \left(4 \frac{d^2 i_L}{dt^2} \right)$$


$$2 = \frac{1}{5} \frac{d^2 i_L}{dt^2} + 4 \frac{di_L}{dt} + i_L \Rightarrow \boxed{\frac{d^2 i_L}{dt^2} + 20 \frac{di_L}{dt} + 5 i_L = 10}$$

(b)

Initial condition:

$$i_L(0) = \frac{20V}{10\Omega} = 2A$$

$$v_c(0) = 4V$$

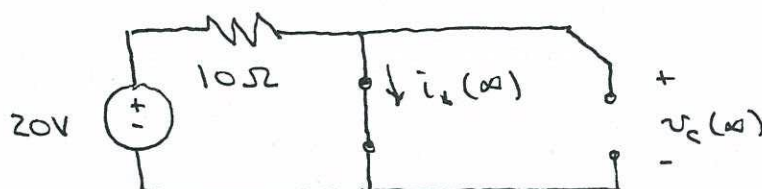
Final condition:

$$v_c(t \rightarrow \infty) = 0V$$

$$i_L(t \rightarrow \infty) = \frac{20V}{10\Omega} = 2A$$

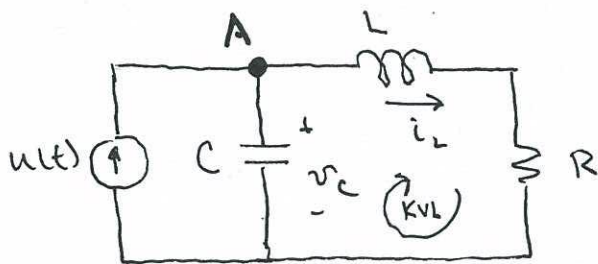8.5

For generic R, L, C : (we'll plug in specific values later)



- (a) Defining unknowns v_c, i_L as shown & applying KVL & KCL:

$$\text{KCL at A: } u = C \frac{dv_c}{dt} + i_L$$

$$\text{KVL, right loop: } v_c = L \frac{di_L}{dt} + R i_L$$

$$u = \frac{d^2 i_L}{dt^2} + \frac{R}{L} \frac{di_L}{dt} + \frac{1}{LC} i_L$$

with $R = 4\Omega, L = 1\text{H}, C = 0.01\text{F}$ & noting that $i = i_L$:

$$100u = \frac{d^2 i_L}{dt^2} + 4 \frac{di_L}{dt} + 100 i_L$$

- (b) From coefficients of differential equation of part (a):

$$\omega_n = \sqrt{100} = 10 \text{ rad/sec}$$

$$2\zeta\omega_n = 4 \Rightarrow 2\zeta(10) = 4 \Rightarrow \zeta = \frac{4}{20}$$

$$\left. \begin{array}{l} \omega_n = 10 \text{ rad/s} \\ \zeta = 0.2 \end{array} \right\} \Rightarrow \boxed{\begin{array}{l} \omega_n = 10 \text{ rad/s} \\ \zeta = 0.2 \end{array}}$$

↓ continued

8.5 (cont'd)

(c)


$$M_p \approx 1 - \frac{\zeta}{0.6} = 1 - \frac{0.2}{0.6}$$

$\zeta = 0.2$ From part (a)

$$\underline{M_p = 0.67}$$

steady-state response:

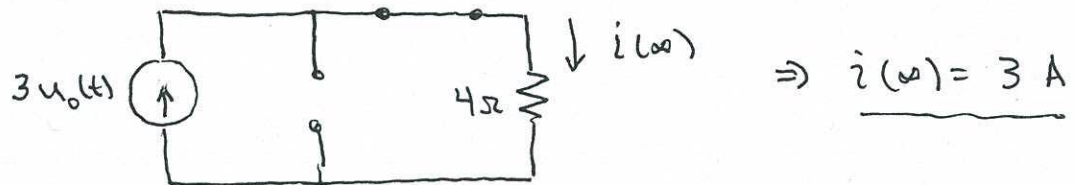Circuit as $t \rightarrow \infty$, with $u(t) = 3u_0(t)$ A:



Maximum value:

$$i_{\max} = 3A + 0.67(3A)$$

$$\boxed{i_{\max} = 5A}$$

8.6

$$\frac{d^2 i(t)}{dt^2} + 6 \frac{di(t)}{dt} + 100 i(t) = 50 u_0(t)$$

$$(a) \quad \omega_n = \sqrt{100} \Rightarrow \boxed{\omega_n = 10 \text{ rad/sec}}$$

$$2\zeta\omega_n = 6 \Rightarrow \zeta = \frac{6}{2(10)} \Rightarrow \boxed{\zeta = 0.3}$$

$$\omega_d = \omega_n \sqrt{1-\zeta^2} = 10\sqrt{1-0.3^2} \Rightarrow \boxed{\omega_d = 9.54 \text{ rad/s}}$$


(b) Determine steady-state response, t_r , maximum value:

steady-state response (from diff. eqn):


$$\cancel{\frac{d^2 i_{ss}}{dt^2}} + 6 \cancel{\frac{di_{ss}}{dt}} + 100 i_{ss} = 50 \Rightarrow i_{ss} = \frac{50}{100} = 0.5 \text{ A}$$

$$M_p \approx 1 - \frac{\zeta}{0.6} = 1 - \frac{0.3}{0.6} = 0.5 \Rightarrow i_{\text{peak}} = 0.75 \text{ A}$$
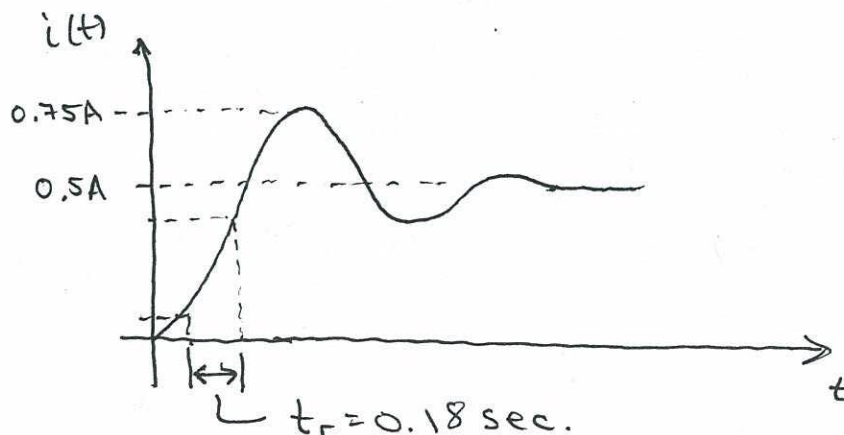
$$t_r \approx \frac{1.8}{\omega_n} = 0.18 \text{ sec}$$



8.7

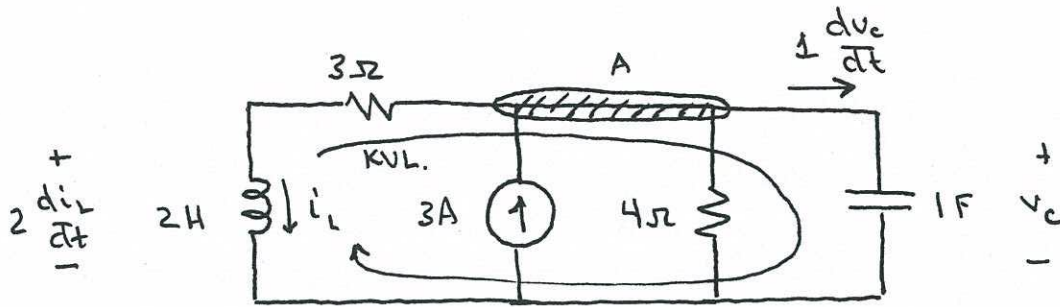(a) circuit for $t > 0$:

KCL, node A: $3A = i_L + \frac{v_C}{4\Omega} + \frac{dv_C}{dt}$


KVL, loop shown: $2 \frac{di_L}{dt} + 3i_L = v_C$

$$\frac{dv_C}{dt} = 2 \frac{d^2 i_L}{dt^2} + 3 \frac{di_L}{dt}$$

Substituting:


$$3A = i_L + \frac{1}{4} \left[2 \frac{di_L}{dt} + 3i_L \right] + \left[2 \frac{d^2 i_L}{dt^2} + 3 \frac{di_L}{dt} \right]$$

$$2 \frac{d^2 i_L}{dt^2} + \frac{7}{2} \frac{di_L}{dt} + \frac{7}{4} i_L = 3$$

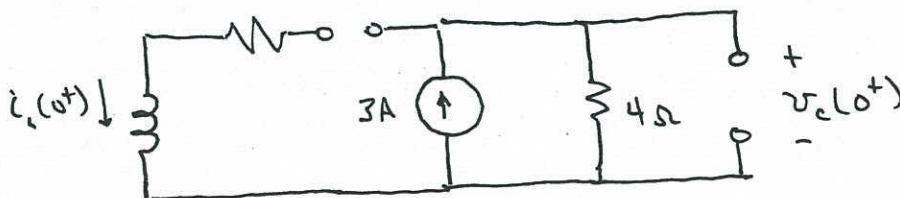(b) $t = 0^-$:

$$i_L(0) = 0A$$


$$v_C(0) = 12V$$

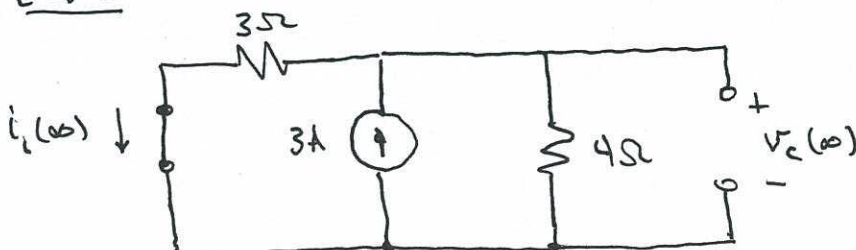 $t \rightarrow \infty$:

$$i_L(\infty) = \frac{12}{7}A$$

$$v_C(\infty) = \frac{36}{7}V$$

8.8

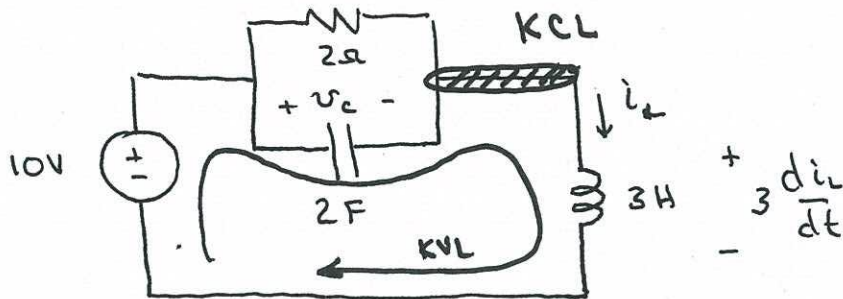(a) circuit for $t > 0$ 


KVL as shown: $10V = v_c + 3 \frac{di_L}{dt}$

KCL as shown: $\frac{v_c}{2\Omega} + (2F) \frac{dv_c}{dt} = i_L \Rightarrow \frac{di_L}{dt} = 2 \frac{d^2 v_c}{dt^2} + \frac{1}{2} \frac{dv_c}{dt}$

Substituting:

$$10V = v_c + 3 \left[2 \frac{d^2 v_c}{dt^2} + \frac{1}{2} \frac{dv_c}{dt} \right]$$


$$10 = v_c + \frac{3}{2} \frac{dv_c}{dt} + 2 \frac{d^2 v_c}{dt^2}$$

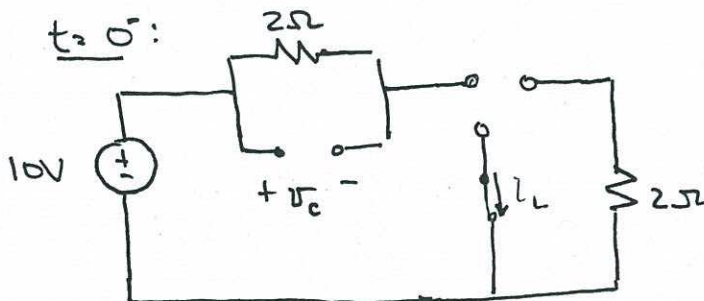(b) $t = 0^-$:

$$v_c(0^+) = v_c(0^-) = 10V \left(\frac{2\Omega}{2\Omega + 2\Omega} \right)$$

$$v_c(0^+) = 5V$$


$$i_L(0^+) = 0A$$

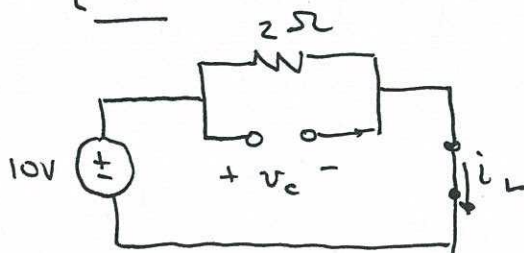 $t \rightarrow \infty$ 

$$v_c(t \rightarrow \infty) = 10V$$

$$i_L(t \rightarrow \infty) = \frac{10V}{2\Omega} = 5A$$

8.9

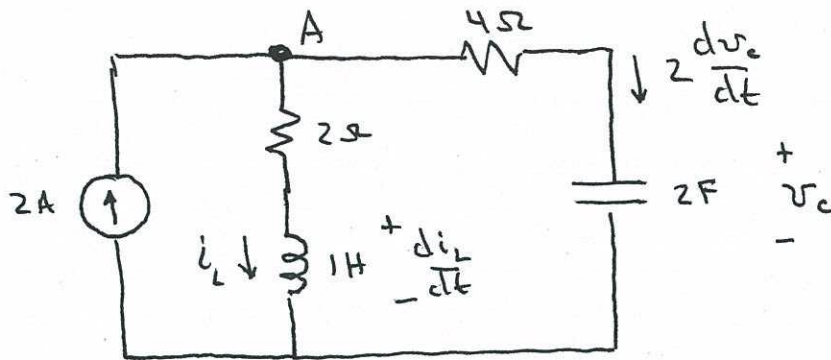(a) Circuit for $t > 0$:

KCL at A: $2A = i_L + 2 \frac{dv_c}{dt}$ (*)


KVL, right loop: $\frac{di_L}{dt} + 2i_L = 4\Omega \left(2 \frac{dv_c}{dt}\right) + v_c$ (**)

From (*), $i_L = 2 - 2 \frac{dv_c}{dt}$ $\Rightarrow \frac{di_L}{dt} = -2 \frac{d^2v_c}{dt^2}$


Substituting into (**):

$$-2 \frac{d^2v_c}{dt^2} + 2 \left[2 - 2 \frac{dv_c}{dt}\right] = 8 \frac{dv_c}{dt} + v_c$$

$$4 = 2 \frac{d^2v_c}{dt^2} + 12 \frac{dv_c}{dt} + v_c$$

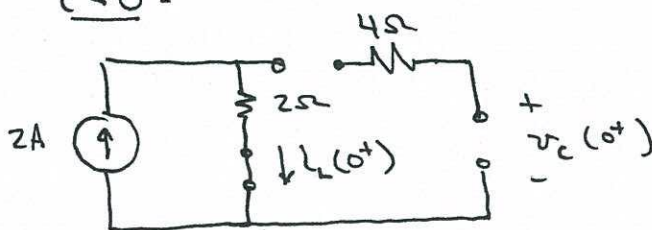(b) $t \leq 0$:

$$\begin{aligned} i_L(0) &= 2A \\ v_c(0) &= 0V \end{aligned}$$

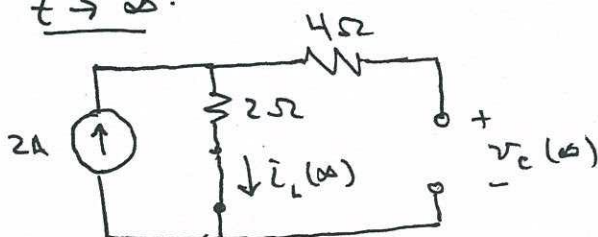 $t \rightarrow \infty$:

$$\begin{aligned} i_L(\infty) &= 2A \\ v_c(\infty) &= 4V \end{aligned}$$

8.10

Put differential equation in standard form (divide by 2):

$$\frac{d^2 v_{out}}{dt^2} + 2 \frac{dv_{out}}{dt} + 25 v_{out} = 50 v_{in}$$

$$\omega_n^2 = 25 \Rightarrow \omega_n = 5 \text{ rad/sec}$$

$$2\zeta\omega_n = 2 \Rightarrow \zeta = \frac{1}{\omega_n} = 0.2$$

$$M_p \approx 1 - \frac{\zeta}{0.6} = 0.67$$

constant input $\Rightarrow \frac{dv_{out}}{dt} = 0, \frac{d^2 v_{out}}{dt^2} = 0$ as $t \rightarrow \infty$

$$25 v_{out}(t \rightarrow \infty) = 50 v_{in}(t \rightarrow \infty)$$


$$v_{out}(t \rightarrow \infty) = \frac{50}{25} v_{in}(t \rightarrow \infty) = \frac{50}{25} (2V)$$

$$v_{out}(t \rightarrow \infty) = 4V$$

$$v_{out} \Big|_{\max} = v_{out}(t \rightarrow \infty) [1 + M_p] = 4V [1 + 0.67]$$

$$\boxed{v_{out} \Big|_{\max} = 6.67V}$$

8.11

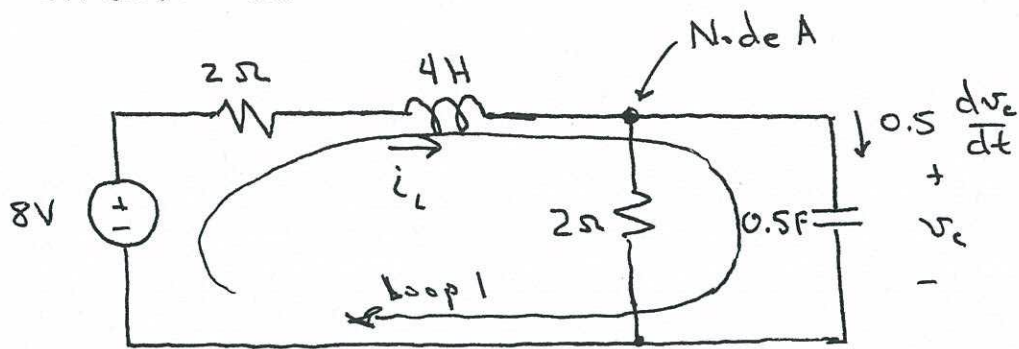Circuit for $t > 0$:

$$\text{KVL, loop 1: } -8V + (2\Omega)i_L + (4H)\frac{di_L}{dt} + v_c = 0$$

$$\text{KCL, Node A: } i_L = \frac{v_c}{2\Omega} + \frac{1}{2} \frac{dv_c}{dt}$$


$$\downarrow \frac{d}{dt}$$

$$\frac{di_L}{dt} = \frac{1}{2} \frac{dv_c}{dt} + \frac{1}{2} \frac{d^2 v_c}{dt^2}$$

Substituting:


$$8 = 2 \left[\frac{v_c}{2} + \frac{1}{2} \frac{dv_c}{dt} \right] + 4 \left[\frac{1}{2} \frac{dv_c}{dt} + \frac{1}{2} \frac{d^2 v_c}{dt^2} \right]$$

$$\boxed{8 = 2v_c + 3 \frac{dv_c}{dt} + 2 \frac{d^2 v_c}{dt^2}}$$

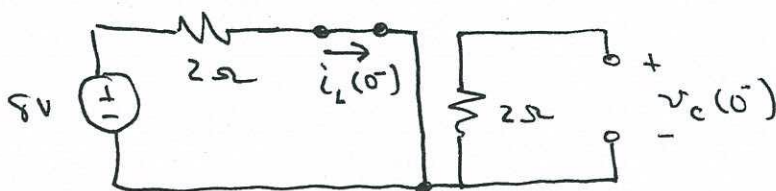(b) $t = 0^-$:

$$v_c(t=0^+) = v_c(0^-) = 0V$$

$$i_L(t=0^+) = i_L(0^-) = 4A$$

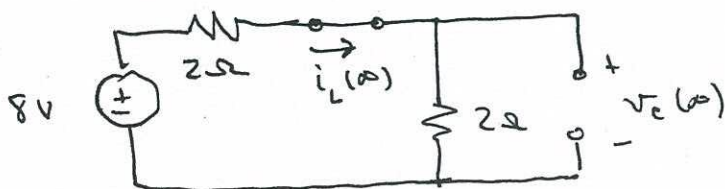 $t \rightarrow \infty$:

$$v_c(t \rightarrow \infty) = 4V$$

$$i_L(t \rightarrow \infty) = 2A$$